

פתרון שאלות הבגרות

באלקטרוניקה תקבילית

לפי נושאים


משנת 2012 עד 2000

הכנת המורה

ותד עבד אלטיף

פתרון שאלות טרנזיסטורים

4 = 100 2012 11/12 2012/2013 JSC

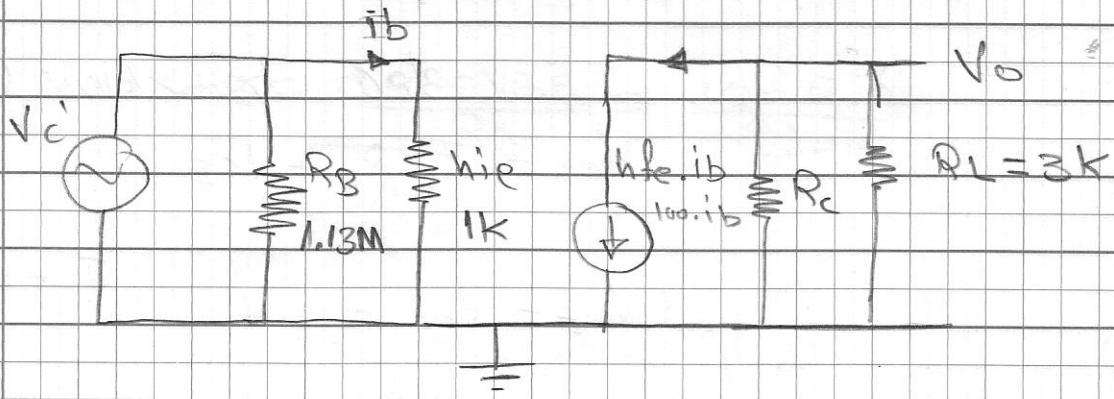

$$A_v = \frac{V_o}{V_i} = -200 = \frac{-h_{fe} \cdot i_b \cdot R_C \parallel R_L}{i_b \cdot h_{ie}}$$

$$-200 = \frac{-100 \cdot R_C \parallel R_L}{1k}$$

$$-200k = \frac{R_C \parallel R_L}{-100}$$

$$2000 = -\frac{R_C \cdot 3k}{R_C + 3k}$$

$$2/R_C + 6000/R_C = R_C/3k$$

$$6000 = R_C = \boxed{6k\Omega}$$

$$I_B = \frac{12 - V_{BE}}{R_B} = \frac{12 - 0.7}{1.13M} = \boxed{10\mu A}$$

$$I_C = \beta \cdot I_B = 100 \times 10\mu A = \boxed{1mA}$$

$$V_{CC} = I_C \cdot R_C + V_{CE}$$

$$12 = 1mA \times 6k + V_{CE}$$

$$12 = 6 + V_{CE}$$

$$V_{CE} = \boxed{6V}$$

8.6/16 300 3M - 20 9/12/22

20/2 mko 4 fcoo pona

3/28 1/ mkoN (E)

$$V_{CC} = I_C \cdot R_C + V_{CE}$$

$$V_{CE} = V_{CC} = 12V$$


$$I_C = 0$$

$$V_{CC} = I_C \cdot R_C$$

$$V_{CE} = 0$$

$$12 = I_C \cdot 6K$$

$$I_C = \frac{12}{6K} = 2mA$$

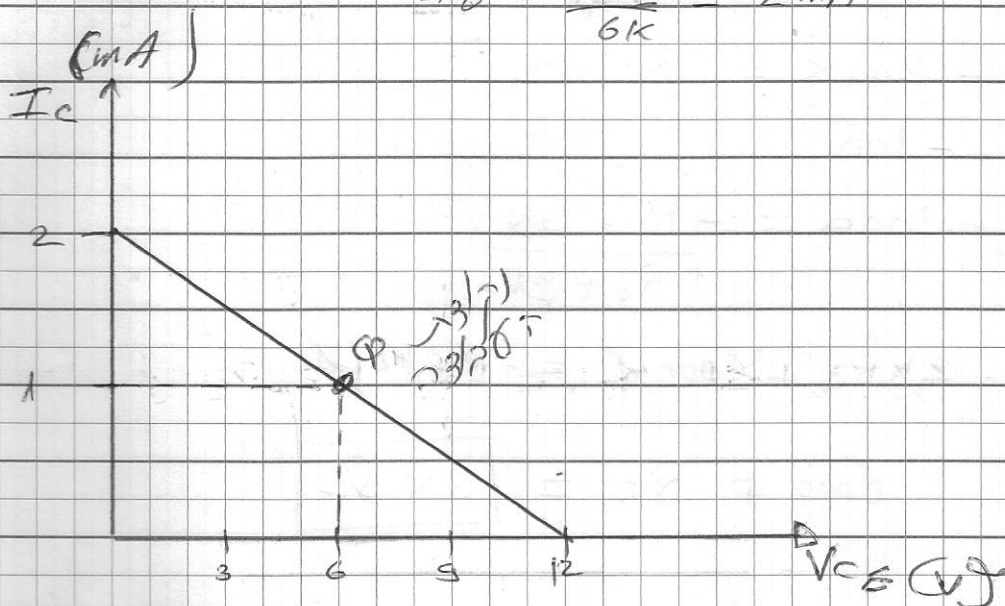

f.c.k 328 3N1 - 20 3/222

4. a) $\sqrt{100}$ 2011 W12ED

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{10 - 0,7}{830K}$$

$$= \boxed{10 \mu A}$$

(K)

$$V_{CC} = I_C \cdot R_C + V_{CE}$$

(2)


$$V_O = \beta \cdot I_B \cdot R_C + 4$$

$$6 = 100 \cdot 10 \mu A \cdot R_C$$

$$R_C = \frac{6}{1 \text{mA}} = \boxed{6 \text{K} \Omega}$$

$$\frac{V_O}{V_i} = \frac{2V}{20mV} = -100$$

(E)

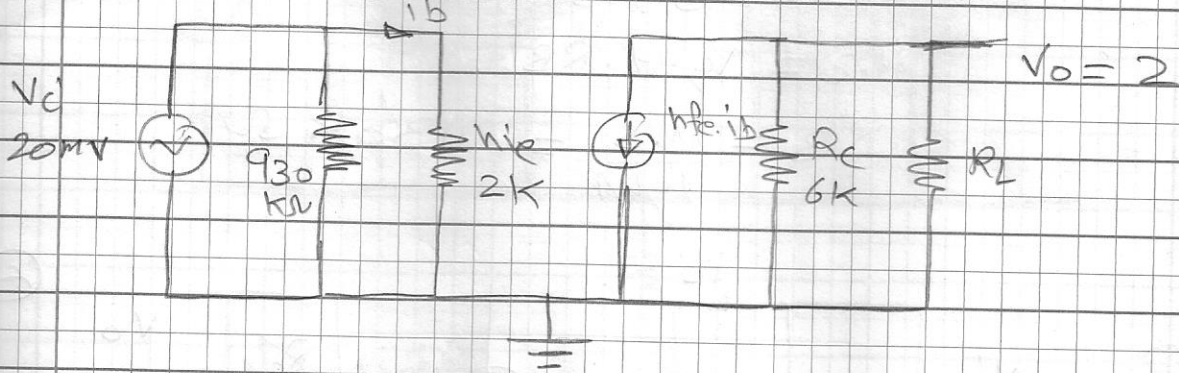

$$\frac{V_O}{V_i} = -100 = \frac{-h_{fe} \cdot I_B \cdot R_C \parallel R_L}{I_B \cdot r_{be}}$$

$$r_{be} \cdot 100 = -100 \cdot R_C \parallel R_L$$

$$2000 = \frac{R_C \cdot R_L}{R_C + R_L} = \frac{6K \cdot R_L}{6K + R_L}$$

$$6000K + 2 \cdot R_L = 6K \cdot R_L$$

$$12000 = 4R_L$$

$$R_L = \boxed{3 \text{K} \Omega}$$

2. 6K 32K 321-27 31222

4.5W $\sqrt{10}$ 2010 W17E2

$$V_{CC} = I_C \cdot R_C + V_{CE}$$

(1)

$$12 = I_C \cdot R_C + V_{CE}$$

120kV

$$I_C = 4mA \quad V_{CE} = 0$$

$$12 = 4mA \cdot R_C$$

$$R_C = \frac{12}{4mA} = \boxed{3k\Omega}$$

$$V_{CE} = 9V$$

120kV

(2)

$$I_C = 1mA$$


$$I_B = 10\mu A$$

$$12 = V_{RB} + V_{BE}$$

$$12 = I_B \cdot R_B + 0.7$$

$$11.3 = 10\mu A \cdot R_B$$
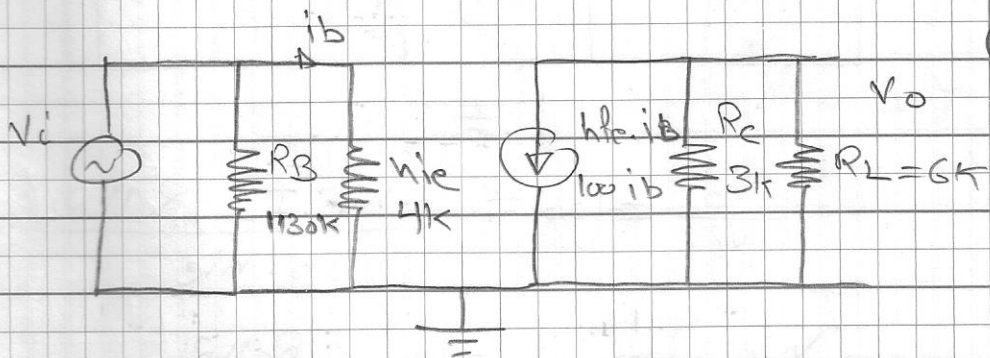
$$R_B = \frac{11.3}{10\mu A} = 1130k\Omega$$



(3)

$$A_v = \frac{-h_{fe} \cdot i_b \cdot R_C \parallel R_L}{i_b \cdot h_{ie}}$$

(3)

$$= \frac{-100 \cdot 3k \cdot 6k}{4k} = \frac{-100 \cdot 2k}{4k} = \boxed{-50}$$

f. G. k. 3. 3. 1 - 2 3. 2. 2

1.6W - 100 2009 - 1.75V

$$V_{CC} = I_B \cdot R_B + V_{BE} \quad (K)$$

$$10 = I_B \cdot 930k + 0,7V$$


$$\frac{9,3V}{930k} = I_B = 10 \mu A$$

$$V_{CC} = I_C \cdot R_C + V_{CE} \quad (2)$$

$$10 = \beta \cdot I_B \cdot R_C + 6V$$

$$4 = 100 \cdot 10 \mu A \cdot R_C$$
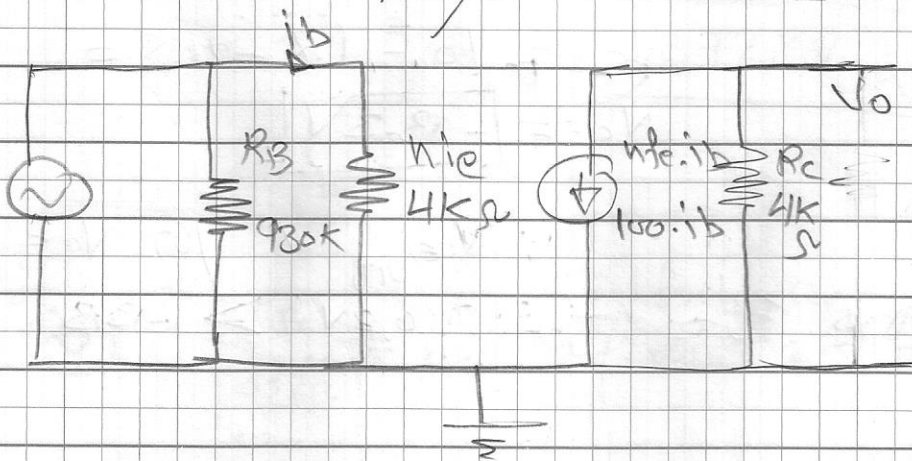
$$R_C = \frac{4}{100 \mu A} = 4k \Omega$$



$$V_o = - \frac{h_{fe} \cdot i_b \cdot R_C}{h_{ie} \cdot i_b} \quad (3)$$

$$= - \frac{100 \cdot 4k}{4k} = -100$$

f. G. b. 300 3M - 20 31000

3.6V 2008 N17C2

$$V_i = I_B \cdot R_B + V_{BE} \quad (K)$$

$$5 = I_B \cdot 20K + 0.7$$

$$I_B = \frac{4.3}{20K} = \boxed{215 \mu A}$$

$$V_{CC} = V_{LED} + V_{RC} + V_{CE} \quad (2)$$

$$10 = 1.8 + 100 \cdot 215 \mu \cdot 1K + V_{CE}$$

$$10 = 1.8 + 21.5 + V_{CE}$$

$$V_{CE} = 10 - 1.8 - 21.5 =$$

$$V_{CE} = \boxed{-13.3V}$$

0.17A 20 p.f

$$V_{CE(sat)} \sim 0.2V > V_{CE} -13.3$$

1.6E 228 311 - 27 3/202

2. En für 2007 17.07

$$V_{CC} = I_C \cdot R_C + V_{CE}$$

$$10 = I_C \cdot 2k + 5V$$


$$I_C = \frac{5}{2k} = \underline{2.5mA}$$

$$V_{CC} = R_B \cdot I_B + V_{BE}$$

$$10 = R_B \cdot \frac{I_C}{\beta} + 0.7$$

$$9.3 = R_B \cdot \frac{2.5mA}{100}$$
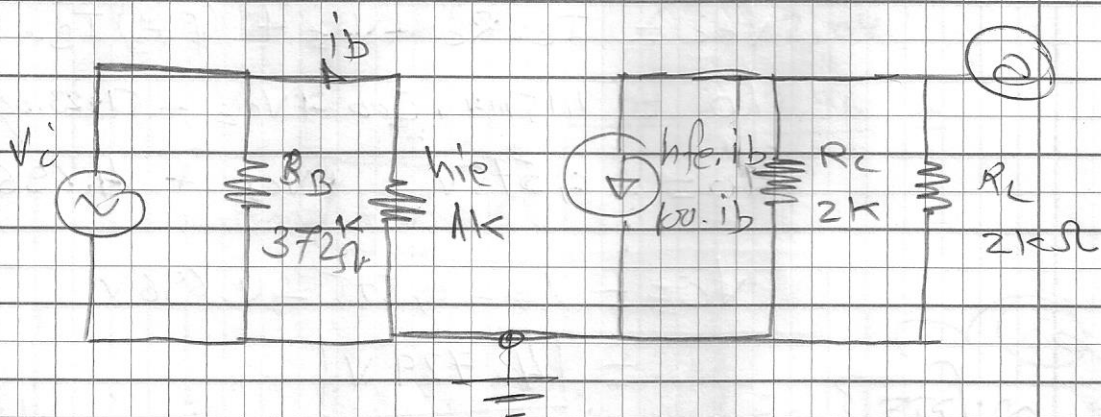
$$R_B = \frac{9.3}{25\mu A} = \underline{372k\Omega}$$



$$\frac{V_o}{V_i} = \frac{h_{fe} \cdot i_b \cdot R_C \parallel R_L}{i_b \cdot h_{ie}}$$

$$= \frac{100 \cdot \frac{2k \cdot 2k}{4k}}{1k}$$

$$= \frac{-100 \cdot 1k}{1k} = \underline{-100}$$

Fig. 3.28 3.28 3.28 3.28 3.28 3.28

4 EN - ke 2008 17EN

$$V_{CC} = I_B \cdot R_B + V_{BE} + I_{RE} \quad (*)$$

$$I_0 = I_B \cdot 200k + 0,7 + (\beta + 1) I_B \cdot 4k\Omega$$

$$9,3 = 200000 I_B + 51 \times 4k I_B$$

$$9,3 = 200000 I_B + 204000 I_B$$

$$I_B = \frac{9,3}{404000} = \boxed{23,02 \mu A}$$

$$I_C = \beta \cdot I_B$$

$$I_C = \boxed{1,15 mA}$$


$$V_{CC} = I_C \cdot R_C + V_{CE} + (\beta + 1) I_B \cdot R_E$$

$$I_0 = 1,15 mA \cdot 500 + V_{CE} + 51 \times 23,02 \mu A \cdot 4k$$

$$I_0 = 0,575V + V_{CE} + 4,696V$$

$$V_{CE} = I_0 - 0,575 - 4,696V$$

$$= \boxed{4,729 V}$$

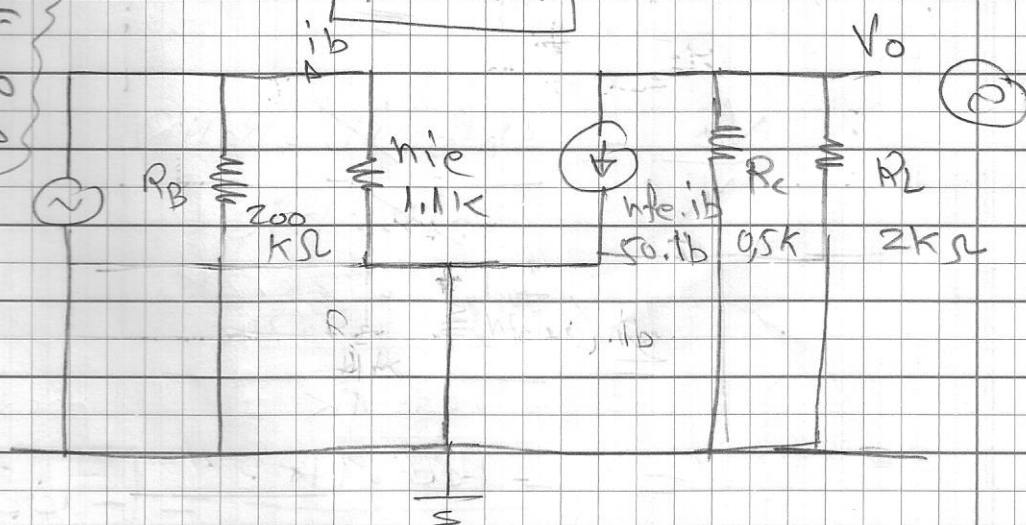

$$\frac{V_o}{V_i} = \frac{-h_{fe} \cdot i_b \cdot R_C \parallel R_L}{i_b \cdot h_{ie}} = \frac{-50 \cdot 0,5k \parallel 2k}{1,1k} = \boxed{-18,18}$$

3 ON $\sqrt{k\Omega}$ 2005 μA μA

$$I_B = \frac{I_C}{\beta} = \frac{2mA}{50} = 40 \mu A$$

(K)

$$V_{CC} = I_B \cdot R_B + 0,7 + (\beta + 1) I_B \cdot R_E$$

$$12 = 40 \mu A \cdot R_B + 0,7 + 51 \times 40 \mu A \cdot 1K$$

$$12 = 40 \mu A \cdot R_B + 0,7 + 2,04$$

$$\frac{12 - 0,7 - 2,04}{40 \mu A} = R_B = \frac{9,26}{40 \mu A}$$

$$\rightarrow R_B = \boxed{231,5 k\Omega}$$


$$V_{CE} = I_C \cdot R_C + V_{CE} + (\beta + 1) I_B \cdot R_E$$

$$12 = 2mA \cdot R_C + 6 + 51 \times 40 \mu A \cdot 1K$$

$$12 = 2mA \cdot R_C + 6 + 2,04$$

$$R_C = \frac{12 - 6 - 2,04}{2mA} = \frac{3,96}{2mA} =$$

$$R_C = \boxed{1980 \Omega}$$

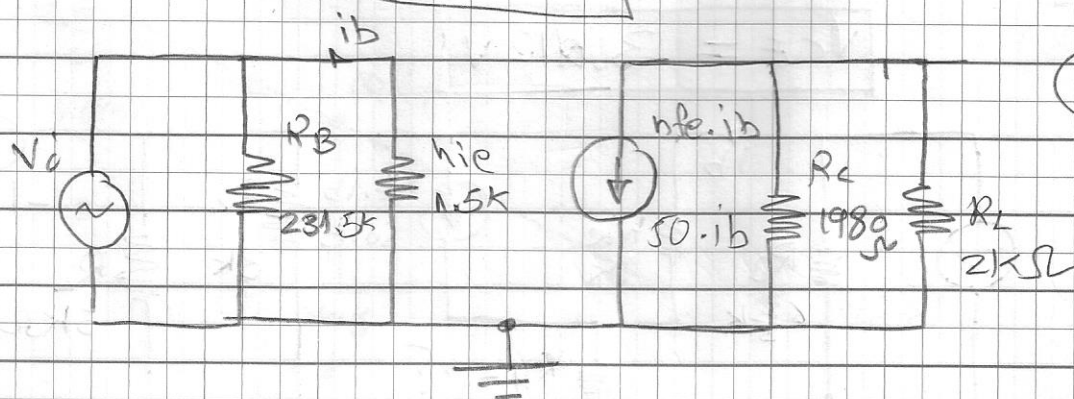

$$A_v = \frac{V_o}{V_i} = \frac{-n h_e i_b \cdot R_C \parallel R_L}{i_b \cdot h_{ie}}$$

$$= -50 \cdot \frac{1980 \cdot 2000}{1980 + 2000}$$

$$= \frac{-50 \cdot 1980 \cdot 2000}{1980 + 2000} = \boxed{-33,16}$$

(L)

Fig. 3.10 BJT-CE amplifier

4. after 2004 when

$$V_B = 12 \cdot \frac{R_2}{R_2 + R_1} = 12 \cdot \frac{10k}{10k + 20k} = 4V \quad (K)$$

$$R_B = R_1 || R_2 = \frac{10k \times 20k}{10k + 20k} = 6\frac{2}{3} k\Omega$$

$$V_B = V_{R_B} + V_{BE} + V_{R_4} + V_{R_5}$$

$$4 = I_B \cdot R_B + 0.7 + (\beta + 1) \cdot I_B (R_4 + R_5)$$

$$4 - 0.7 = 6\frac{2}{3} k I_B + 51 I_B (0.5k + 1k)$$

$$3.3V = 6\frac{2}{3} k I_B + 76.5 k I_B$$

$$3.3V = 83.166 k I_B$$

$$I_B = \frac{3.3}{83.166k} = 39.68 \mu A$$


$$I_C = \beta I_B = 50 \times 39.68 \mu A = 1.984 mA$$

$$V_{CC} = I_C \cdot R_3 + V_{CE} + (\beta + 1) \cdot I_B (R_4 + R_5)$$

$$12 = 1.984 mA \times 3k + V_{CE} + 51 \times 39.68 \mu A \cdot 1.5k$$

$$12 = 5.952 + V_{CE} + 3.035$$

$$V_{CE} = 3.012 V$$

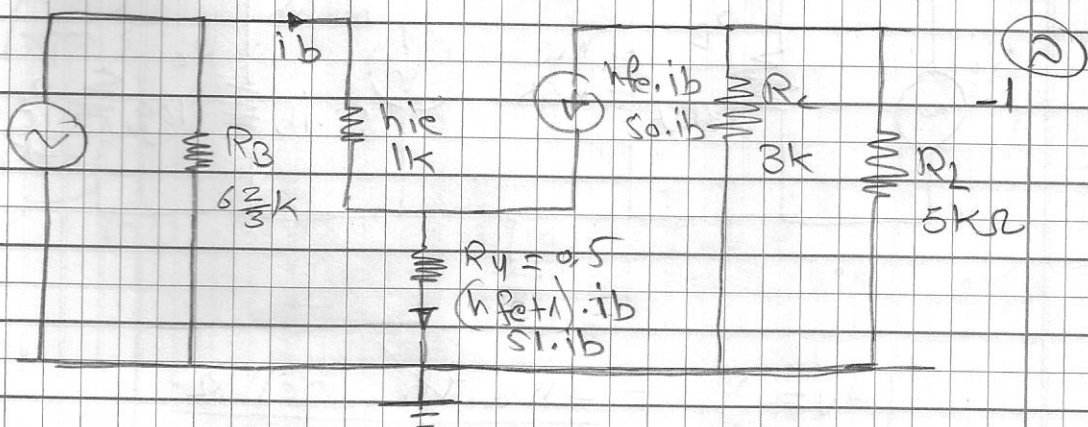

$$\frac{V_o}{V_i} = \frac{-h_{fe} \times R_C || R_L}{h_{ie} + (h_{fe} + 1) R_E} = \frac{-50 \times 3k \times 5k}{1k + 25.5k} = -2$$

$$= \frac{-50 \times 1.875k}{26.5k} = -3.524$$

$$5.326 k \leftarrow R_i = R_B || (h_{ie} + R_E \cdot 51) = \frac{6\frac{2}{3} k \cdot 26.5k}{33.166k}$$

3 ON $\sqrt{k\Omega}$ 2000 μA $\sqrt{V}$

$$V_B = V_{CC} \times \frac{R_2}{R_1 + R_2} = 15 \times \frac{10k}{25k} = 6V \quad (K)$$

$$R_B = R_1 \parallel R_2 = \frac{15k \times 10k}{25k} = 6k\Omega$$

$$V_B = I_B \cdot R_B + V_{BE} + (\beta + 1) I_B \cdot R_E$$

$$6 = I_B \cdot 6k + 0.7 + 51 \cdot 1k \cdot I_B$$

$$5.3 = 56k I_B$$

$$I_B = \frac{5.3}{56k} = 92.98 \mu A$$


$$I_C = 50 \cdot I_B = 4.649 mA$$

$$V_{CC} = I_C \cdot R_C + V_{CE} + (\beta + 1) \cdot I_B \cdot R_E$$

$$15 = 4.649 mA \cdot 1k + V_{CE} + 51 \times 92.98 \mu A \cdot 1k$$

$$15 = 4.649 V + V_{CE} + 4.741 V$$
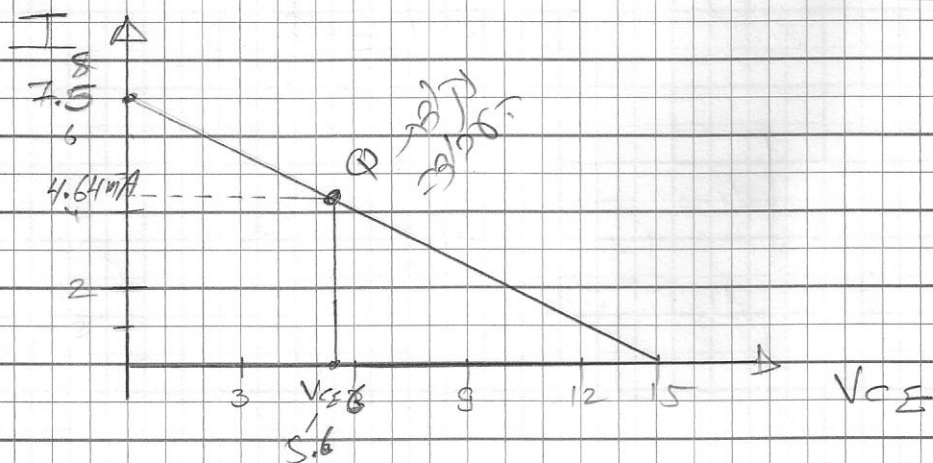
$$V_{CE} = 15 - 4.649 - 4.741 = 5.609 V$$



$$V_{CC} = I_C (R_C + R_E) + V_{CE}$$

$$V_{CE} = 0$$


$$I_C = \frac{15}{2k} = 7.5 mA$$

$$I_C = 0$$

$$V_{CE} = V_{CC} = 15 V$$

Figure 3.1 - 3.12

200 nF 300 pF 100 pF

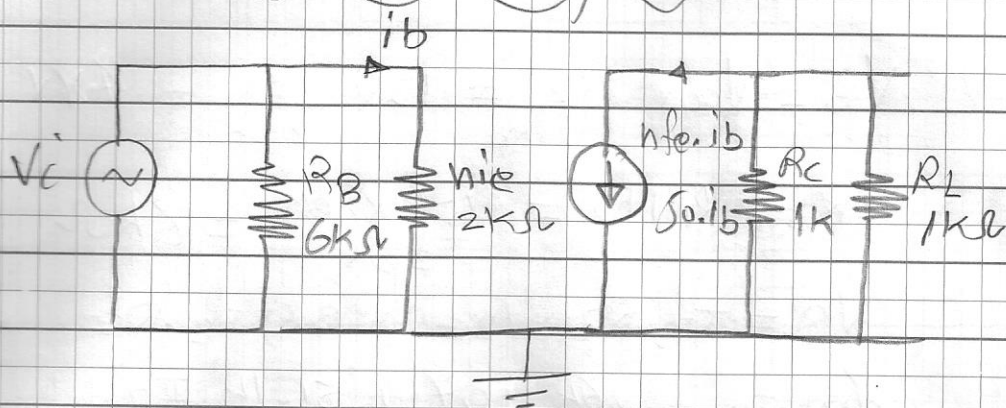

$$\frac{V_o}{V_i} = - \frac{h_{fe} \cdot R_C \parallel R_L}{h_{ie}} = - \frac{50 \times \frac{1k \times 1k}{2k}}{2k}$$

$$= - \frac{50 \times 0.5k}{2k} = \boxed{-12.5}$$

200 nF 300 pF 100 pF