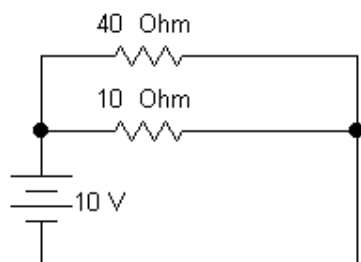



דף עבודה מס' 5 – התנגדות שקולה של מעגל חשמלי

כיתה ט'


חשב התנגדות שקולה של כל אחד מהמעגלים




(3)

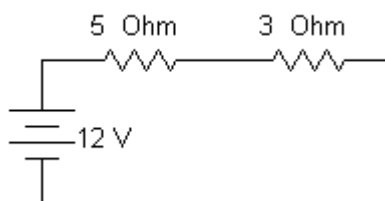


(2)

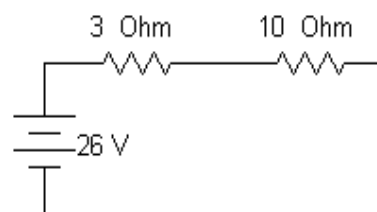


(1)

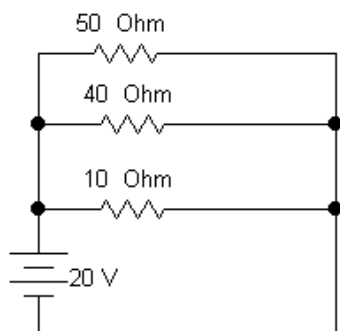


(6)

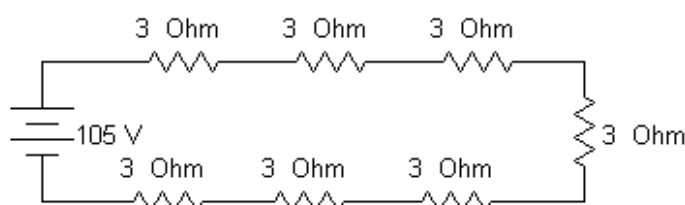


(5)

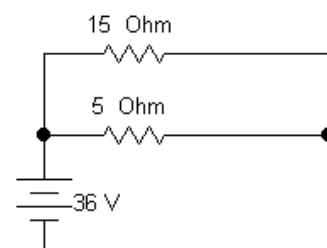


(4)

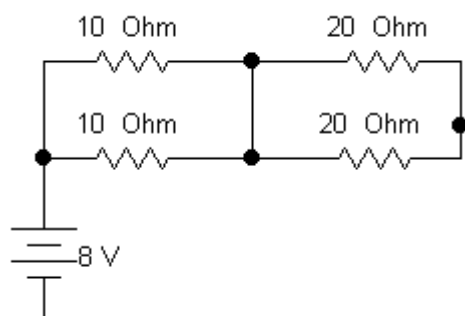


(9)

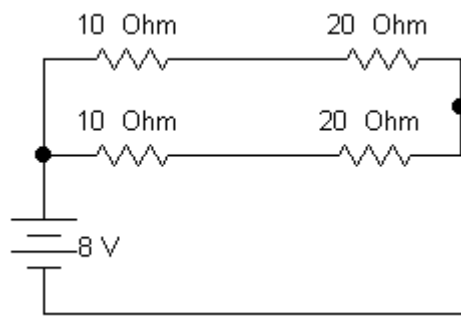


(8)

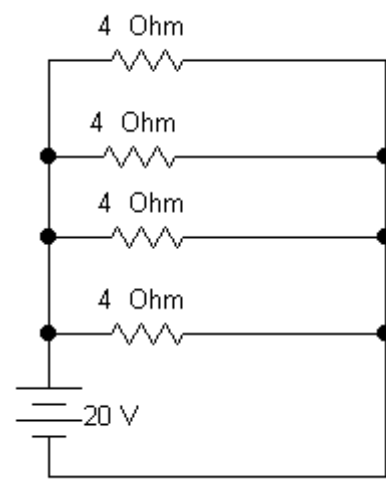

(7)

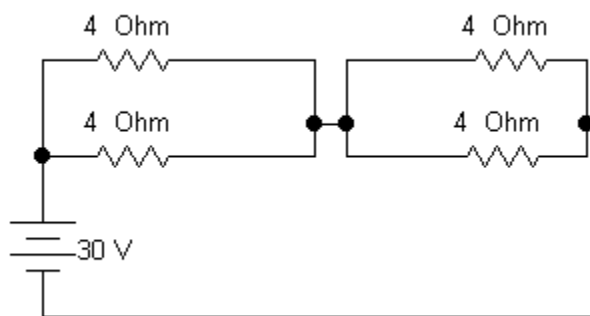

(11)

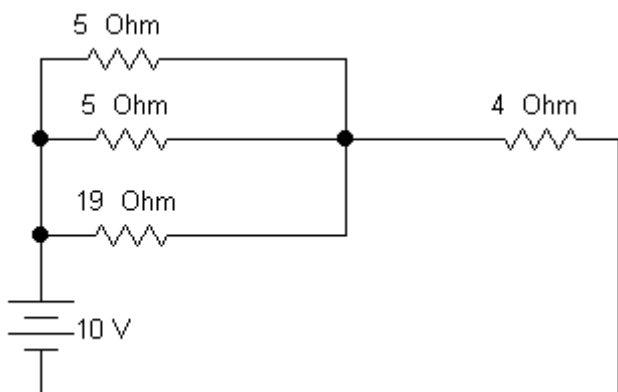

(10)