
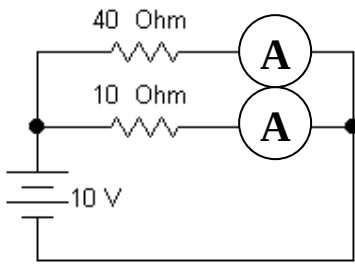



חשב את הזרם הכללי של כל אחד מהמעגלים

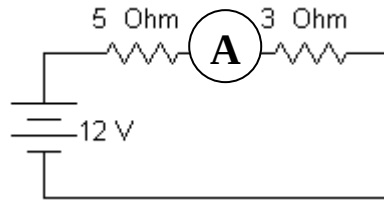


(1)




(2)

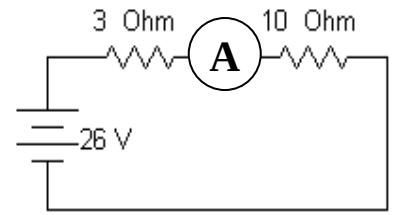


(3)

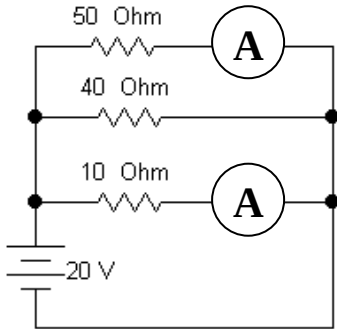


(4)

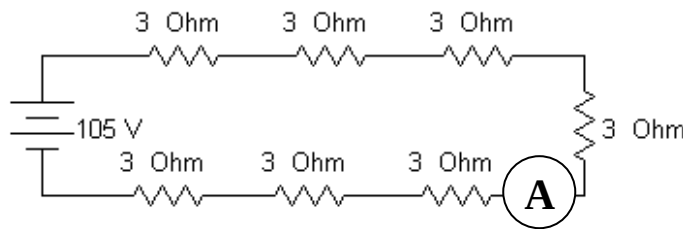


(5)

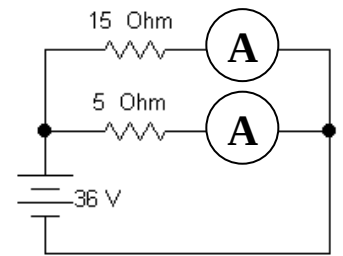


(6)

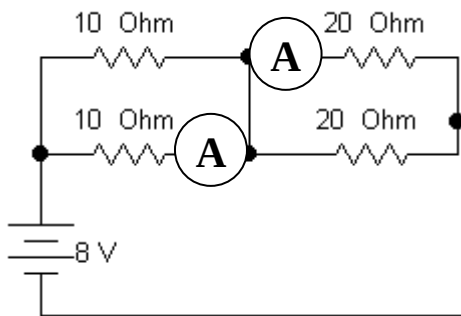


(7)

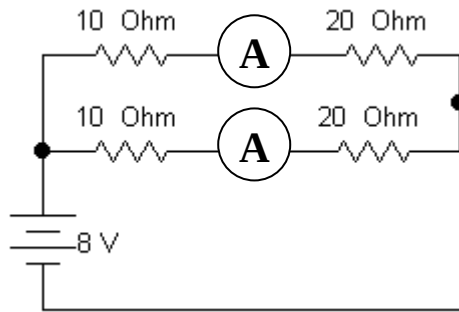


(8)

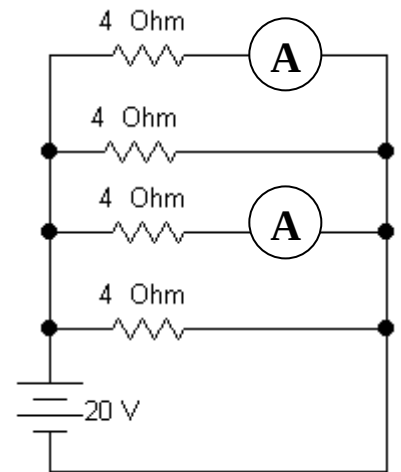

(9)

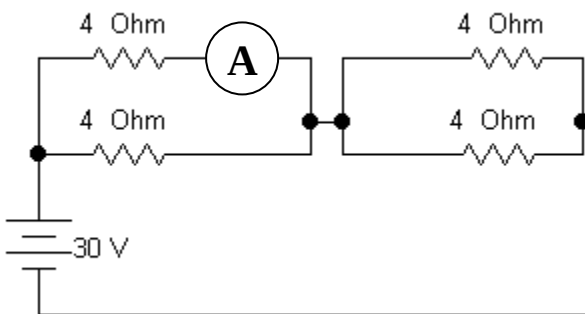

(10)

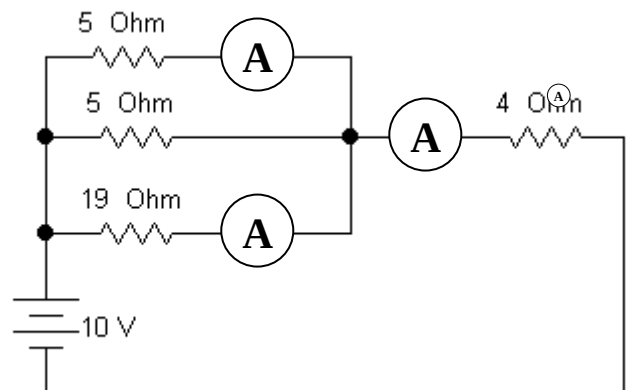

(11)